

## **Midterm Project**

### **Alamein Bank System**

#### **Team Member:**

Mazen mohamed elsayed - 21100912

Abdelrahman Mohamed Abdelaziz – 21100799

Adham Ayman Farouk Ibrahim – 21100782

#### **Supervised by**


**Dr. Ahmed Shalaby**

**Eng. Mariam Boules**

Pin's Names	Type	Description
clk	Input	CLK is used to synchronize all the components
reset	Input	Reset the system
in	Input	Represents the button at the start of the queue
out	Input	Represents the button at the end of the queue
tcount	Input	Represents the number of tellers
Full flag	output	A led that lights up when the queue is full (pcount = 7)
Empty flag	output	A led that lights up when the queue is empty (pcount = 0)
Output Segment Right	output	The wait time could be two digits, in which case they would need to be divided into two seven-segment groups. The seven-segment display on the right (representing the units) is called Output Segment Right.
Output Segment Left	output	The wait time could be two digits, in which case they would need to be divided into two seven-segment groups. The seven-segment display on the left (representing the tenth) is called Output Segment Left.
Output Segment pcount	output	Displays the pcount (0 - 7) on a 7-segment display

Tcount	Pcount	Wtime	BCD
1	0	0	00000000
1	1	3	00000011
1	2	6	00000110
1	3	9	00001001
1	4	12	00010010
1	5	15	00010101
1	6	18	00011000
1	7	21	00100001
2	0	0	00000000
2	1	3	00000011
2	2	4	00000100
2	3	6	00000110
2	4	7	00000111
2	5	9	00001001
2	6	10	00010000
2	7	12	00010010
3	0	0	00000000
3	1	3	00000011
3	2	4	00000100
3	3	5	00000101
3	4	6	00000110
3	5	7	00000111
3	6	8	00001000
3	7	9	00001001

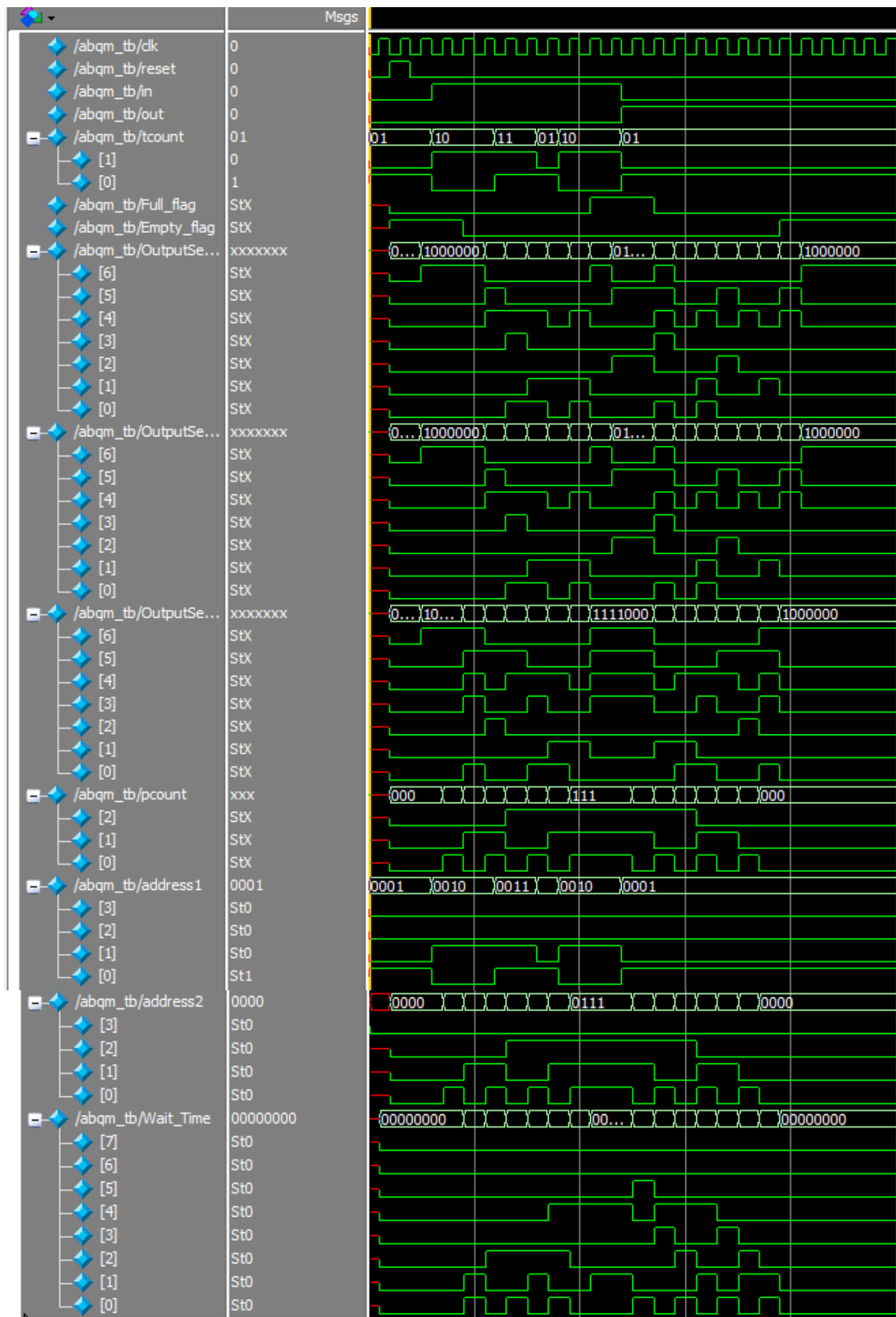This is a Table representing all the possible Pcount – Tcount Combinations and the outputted Wait Time in both Decimal and BCD



## FSM:

